

# Cryptographic implementation using Ferroelectric transistor

Cédric Marchand, Ian O'Connor, Stefan Slesazek, Thomas  
Mikolajick



Journée thématique du GDR



# Agenda

---

1. Introduction
2. Ferroelectric field effect transistor
3. TC-MEM memory and Sbox implementation
4. Non-volatile logic gates and operators for security
5. Conclusion



# Agenda

---

1. Introduction
2. Ferroelectric field effect transistor
3. TC-MEM memory and Sbox implementation
4. Non-volatile logic gates and operators for security
5. Conclusion

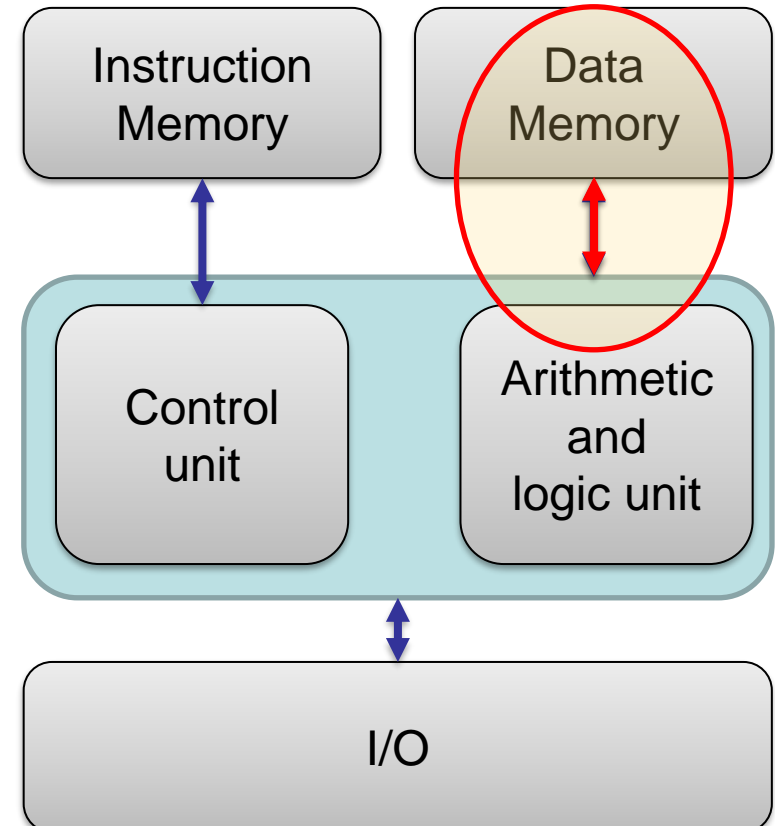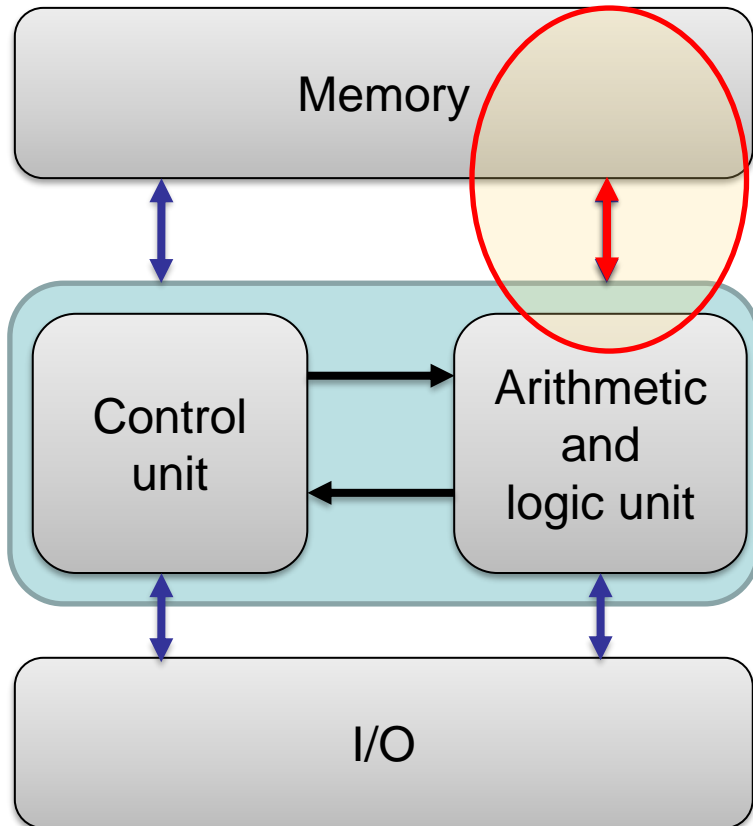
# Context (Classical computing architectures)

- Von Neumann Architecture/ Harvard Architecture
  - Data transfert congestion



Limit performances and energy efficiency

# Sensor node security

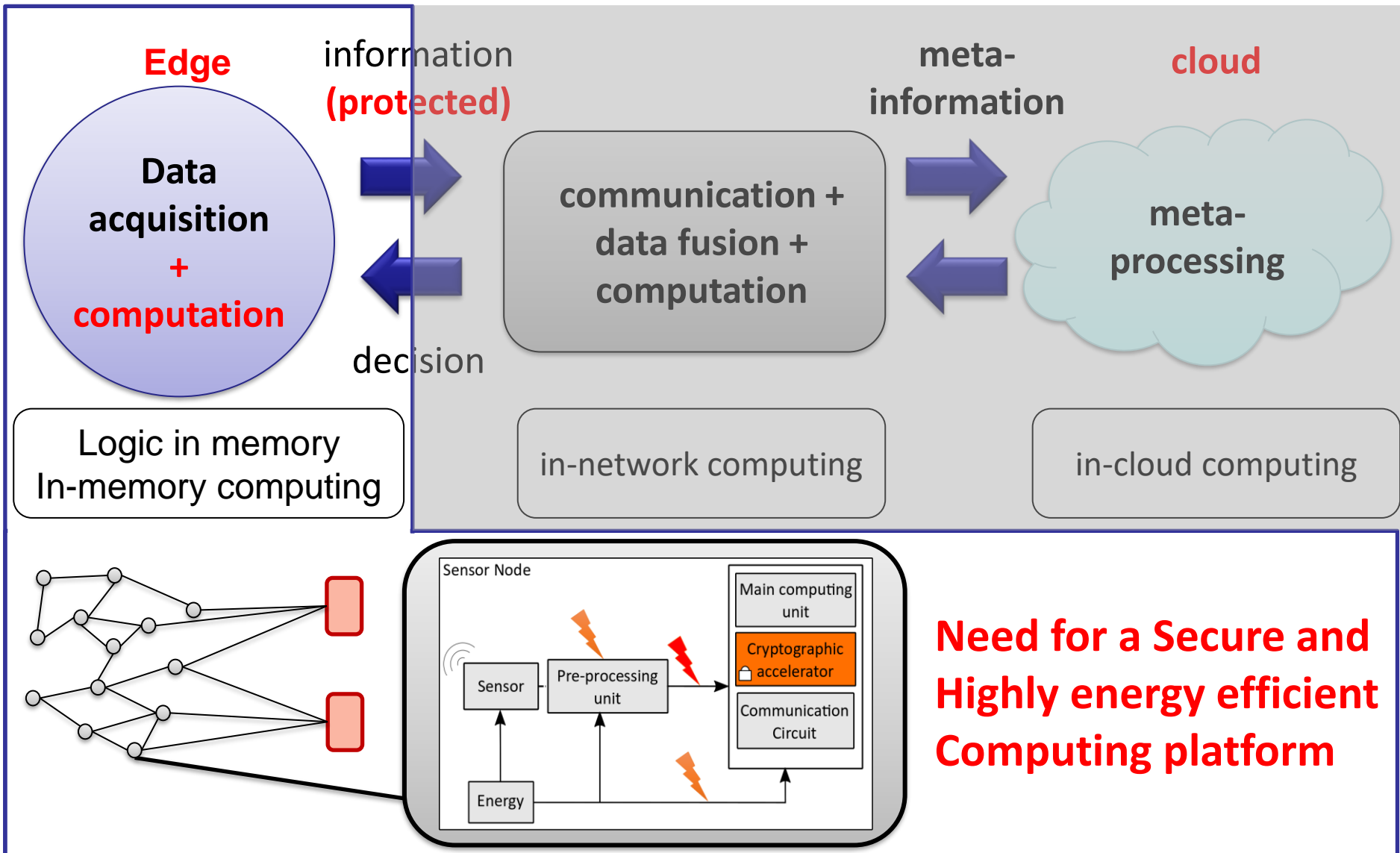


# Non-volatile Opportunities

---

- Emerging and CMOS compatible Non-Volatile memory technologies:
  - New non-volatile logic capabilities
  - Logic in memory
- Opportunity to change the Hardware architectures of computing unit to include Non-Volatile structures:
  - Memory array with computing capabilities
  - Programmable logic gate
  - Custom logic operation with non-volatile operand(s)
- Concept of near-sensor cryptography using non-volatile operations in the pre-processing unit
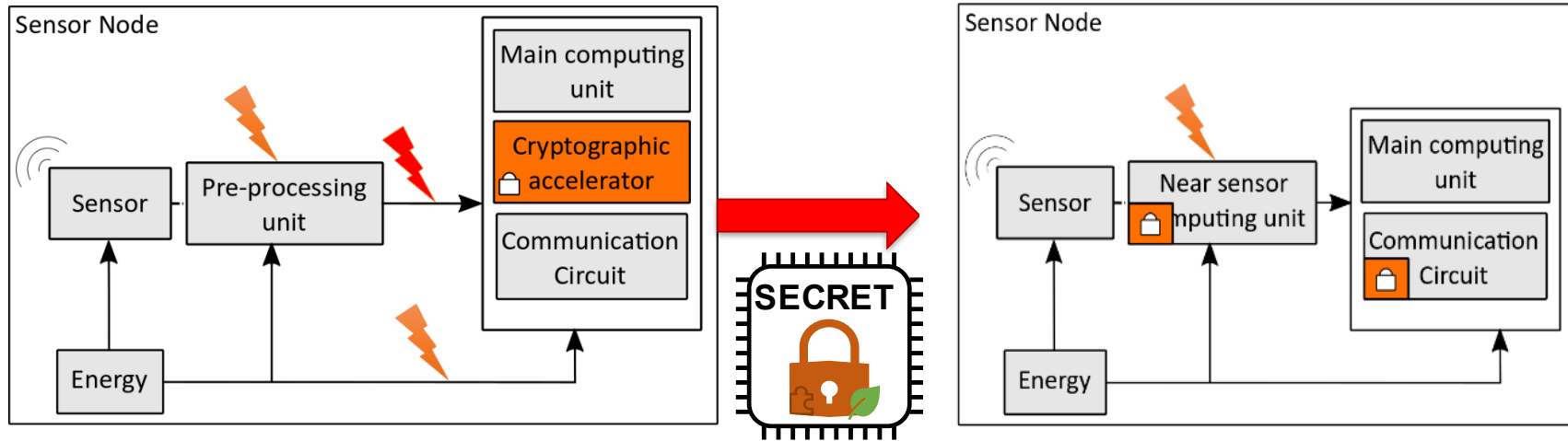
# Non-volatile emerging technologies opportunities



- Add a low-cost security layer in the preprocessing Unit :
  - Use emerging technologies (FeFet for example) to implement part of cryptographic operations inside the preprocessing Unit (Sbox, constant matrix multiplication, ...)
- **In-Memory-Computing** can play a role
- Emerging **TCAM** design → possibility to create a hybrid memory (TCAM **and** MEM) : the TC-MEM



# Agenda

---

1. Introduction
2. Ferroelectric field effect transistor
3. TC-MEM memory and Sbox implementation
4. Non-volatile logic gates and operators for security
5. Conclusion







# Ferroelectric Field Effect Transistor

  

 
 
 
 
# FeFET : single transistor characteristics

FeFET dimension:  
 $W = 500 \text{ nm}$   
 $L = 500 \text{ nm}$


    
# FeFET : single transistor characteristics

FeFET dimension:  
 $W = 500 \text{ nm}$   
 $L = 500 \text{ nm}$





# Agenda

---

1. Introduction
2. Ferroelectric field effect transistor
3. TC-MEM memory and Sbox implementation
4. Non-volatile logic gates and operators for security
5. Conclusion
  
# TC-MEM

- New design bloc:
  - TCAM : Ternary content addressable memory
  - MEM: classical memory addressable by address




<sup>1</sup> X. Yin, K. Ni, D. Reis, S. Datta, M. Niemier and X. S. Hu, "An Ultra-Dense 2FeFET TCAM Design Based on a Multi-Domain FeFET Model," in *IEEE Transactions on Circuits and Systems II: Express Briefs*, vol. 66, no. 9, pp. 1577-1581, Sept. 2019, doi: 10.1109/TCSII.2018.2889225.

<sup>2</sup> C. Marchand, I. O'Connor, M. Cantan, E. T. Breyer, S. Slesazek and T. Mikolajick, "A FeFET-Based Hybrid Memory Accessible by Content and by Address," in *IEEE Journal on Exploratory Solid-State Computational Devices and Circuits*, vol. 8, no. 1, pp. 19-26, June 2022, doi: 10.1109/JXCDC.2022.3168057.

# TC-MEM


- $M = 0$  : Memory mode

 

- When the bit is read,  $V_1 = 1 \Rightarrow V_o = \overline{1 \cdot \bar{S}} = S$


# TC-MEM

- $M = 1$  : TCAM mode

 

$$V_{out} = \overline{V_0 \cdot S} \cdot \overline{V_1 \cdot \bar{S}}$$


# TC-MEM (chip measurement)

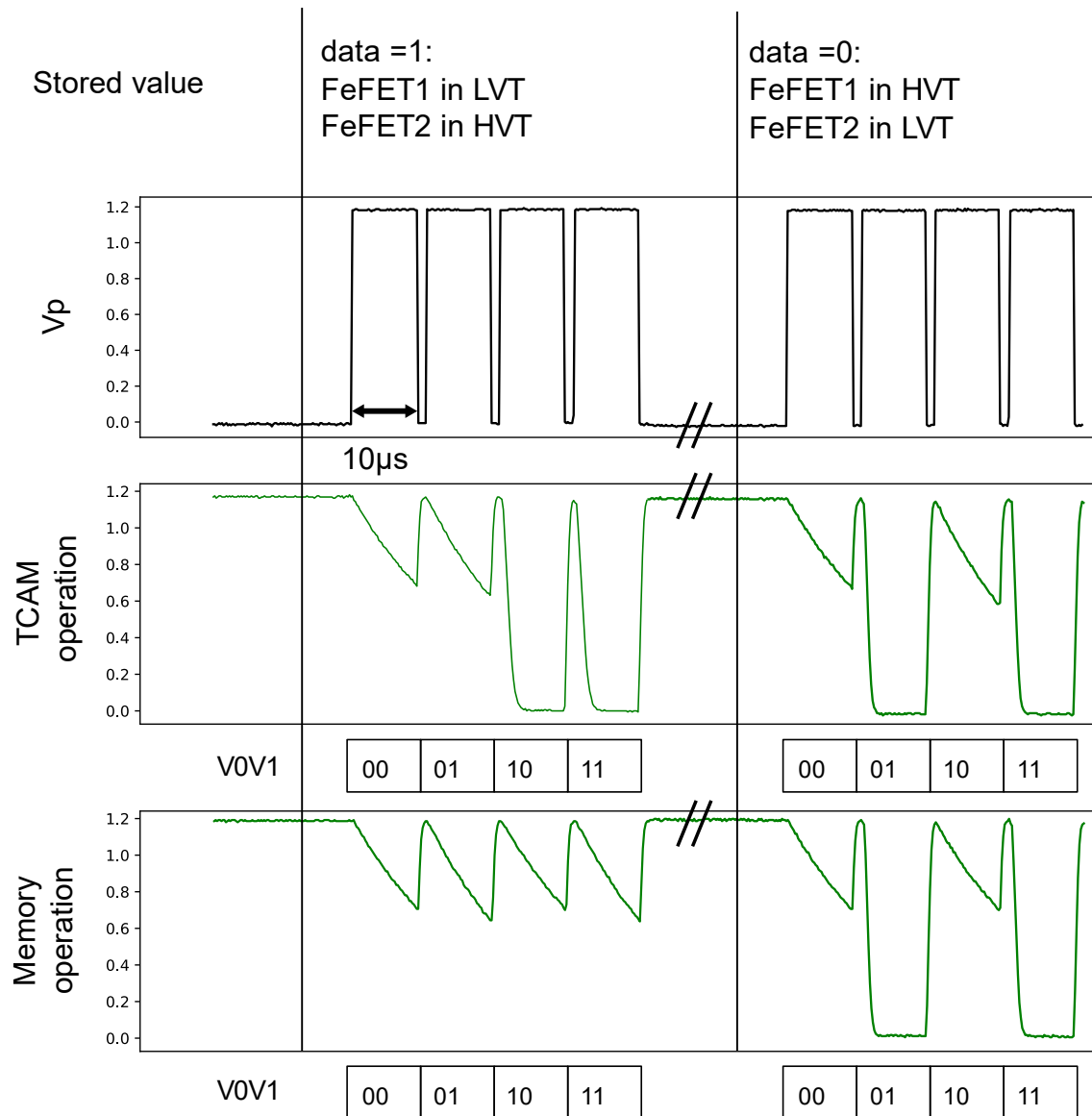



# TC MEM 1<sup>st</sup> generation

- TC MEM 2bit






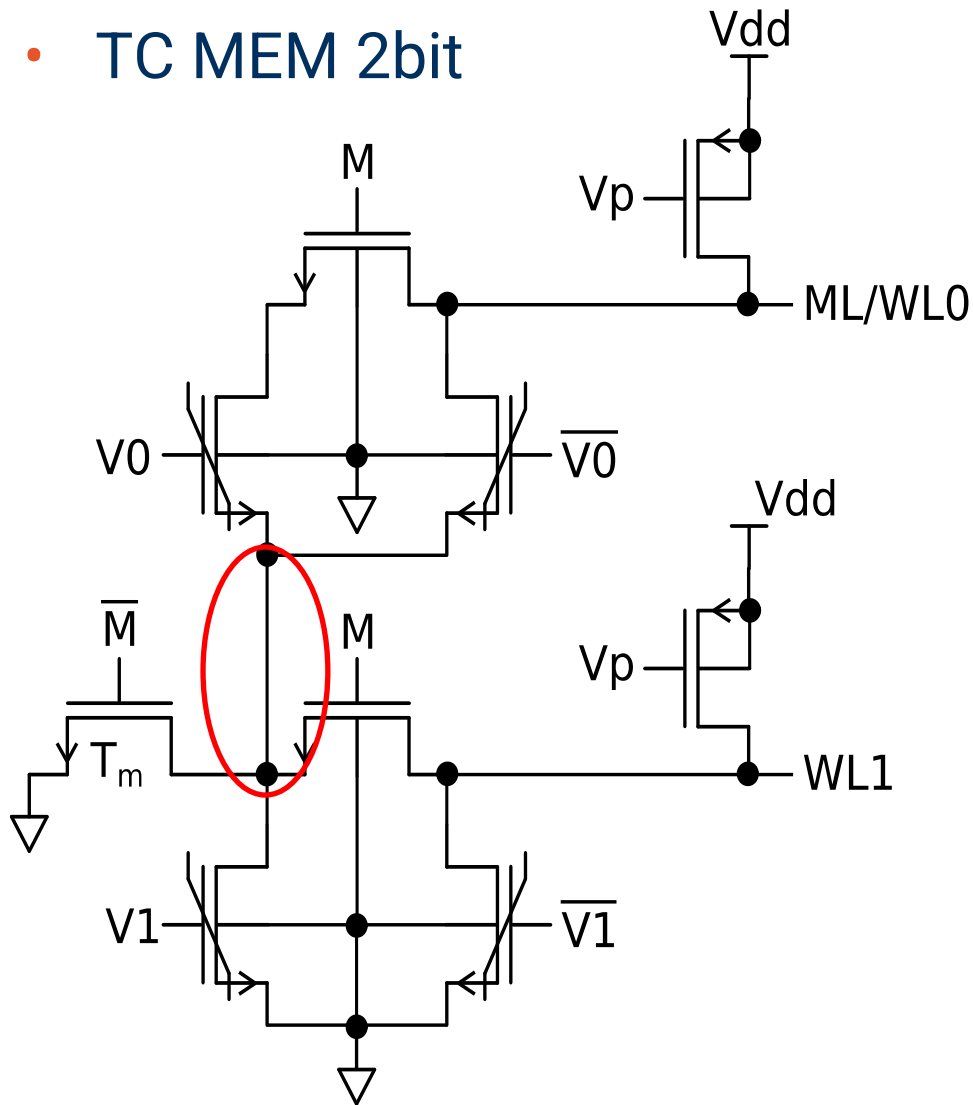


Serial connection problem :

- Programming in TCAM mode:
  - Left FeFET powered
  - Upper FeFET connected to  $V_{dd}$  from drain and source
- Consequence :
  - The upper left FeFET remains un-program in some cases.
- Possible solution :
  - Bring a possible separation between the bitcell.
      
# TC MEM 1<sup>st</sup> generation

- Cannot program  $FeFET_0$  (connected to  $V_0$ )






$$A_0A_1 = 00$$




$$A_0A_1 = 01$$
   
# TC MEM 1<sup>st</sup> generation

- Cannot program  $FeFET_0$  (connected to  $V_0$ )




0,7

   

$$A_0A_1 = 10$$

$$A_0A_1 = 11$$

# TC MEM 2<sup>nd</sup> generation

 


New scaling circuit :

- Programming the bitcells:
  - TCAM Mode
  - $T=1$  and  $C=0$
- Ensure disconnected bitcells and proper programming
- Existence of forbidden state:
  - $M = T = C = 0$
  - $M = 1, T = C = 0$
  - $M = 0, T = C = 1$
  - $M = T = C = 1$

} Floating node

} Possible but useless
- $T = \bar{C}$
- 4 remaining utilizations :
  - Memory
  - TCAM
  - Bitwise Xor
  - Memory with connected bits ?

# TC MEM other solutions

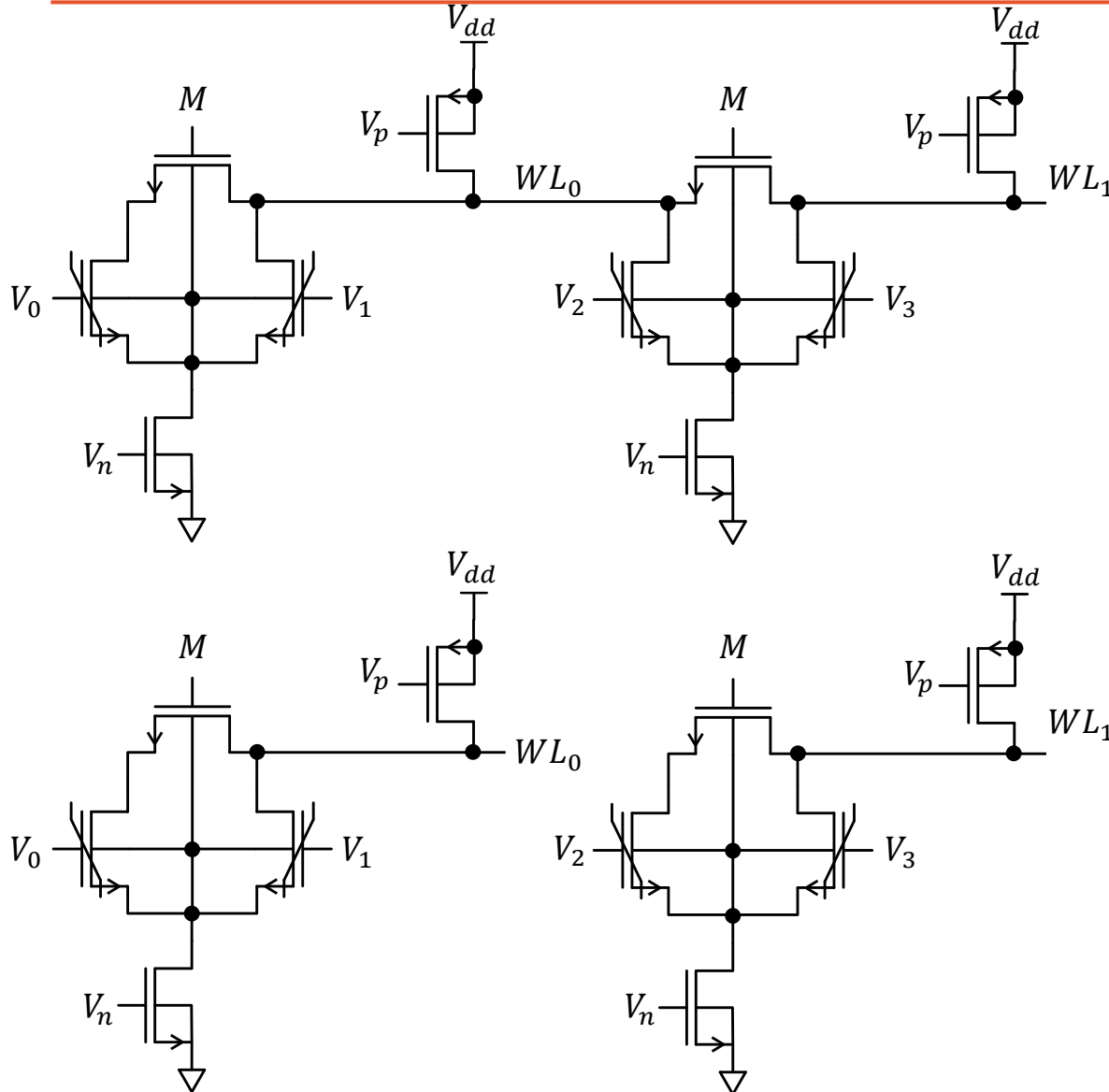


Parallely connected:

- Global match
- No limit in size ?
- More difficult to read in memory
- fewer functionality


Fully separated:

- No global match
  - Bigger output circuit
- No limit in size ?
- All functionality are possible


# Memory mode : 2-bit fully separated

 
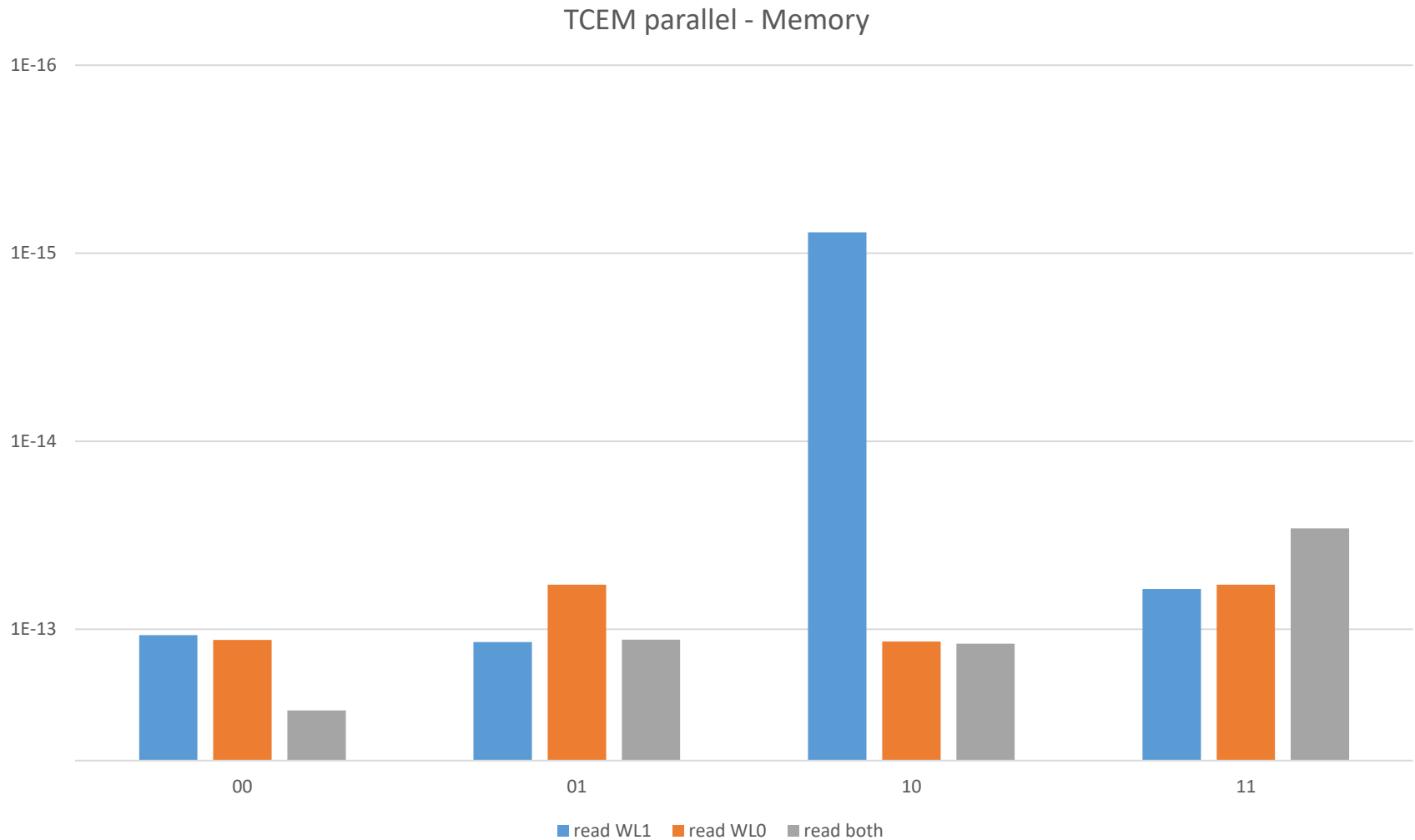
# Memory mode : 2-bit parallelly connected




# Memory mode : 2-bit serially connected

 





# TCAM mode : 2-bit fully separated

 

# TCAM mode : 2-bit parallelly connected

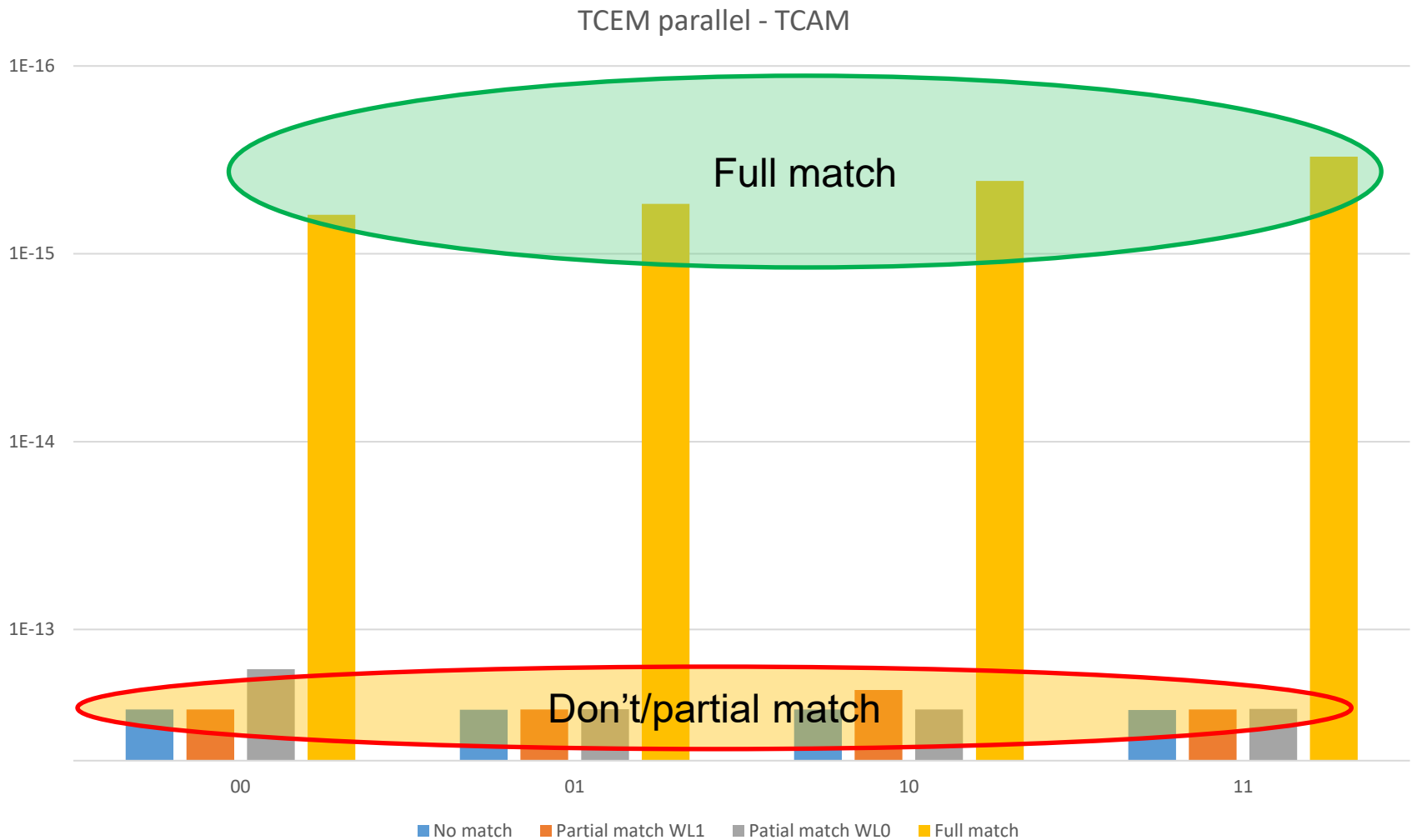

# TCAM mode : 2-bit serially connected

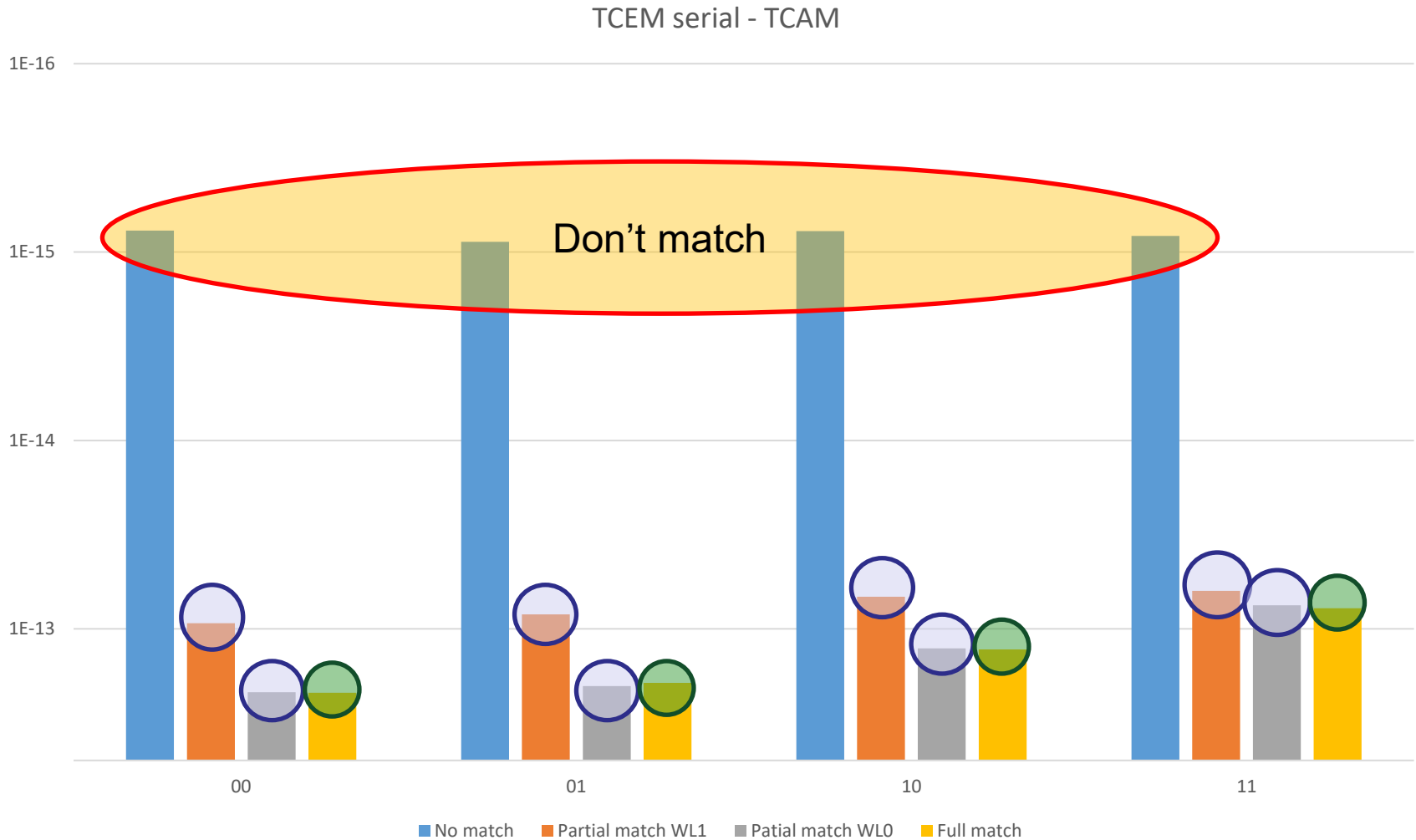

● Full match

● Partial match

# Comparison and discussion


## Memory Mode

Circuit	HW 0	HW 1	HW 2	HW dependency	Order
2-bit separated	$2,70e^{-13}$	$1,13e^{-13}$	$2,89e^{-16}$	Yes	3
2-bit parallel	$2,71e^{-13}$	$1,17e^{-13}$	$2,91e^{-14}$	Yes	1
2-bit serial	$3,63e^{-13}$	$2,22e^{-13}$	$9,59e^{-14}$	Yes	<1

## TCAM Mode

Circuit	No match	Partial Match WL1	Partial Match WL0	Full Match	Dependency
2-bit separated	$4,04e^{-16}$	$1,05e^{-13}$	$9,67e^{-14}$	$2,59e^{-13}$	+ (<1)
2-bit parallel	$2,68e^{-13}$	$2,53e^{-13}$	$2,40e^{-13}$	$4,69e^{-16}$	++ (3)
2-bit serial	$8,11e^{-16}$	$7,69e^{-14}$	$1,55e^{-13}$	$1,55e^{-13}$	-
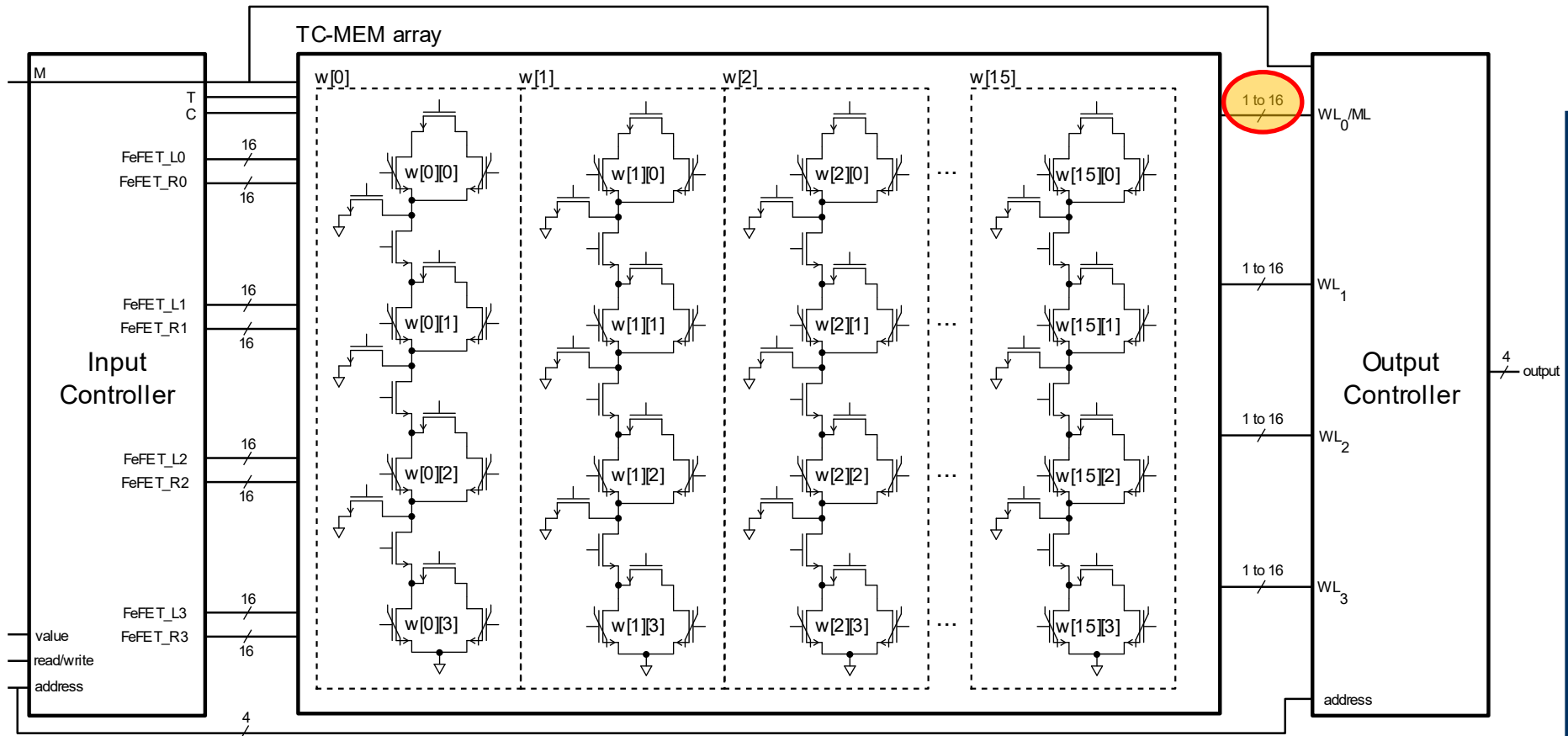
# TC-MEM array (4-bit Sbox implementation)



## Sbox implementation 1:

- Store  $sbox(x)$  in  $w[x]$  for  $x \in \{0; 15\}$ 
  - Encryption  $\rightarrow$  Memory
  - Decryption  $\rightarrow$  TCAM

## Sbox implementation 2:


- Store  $x$  in  $w[sbox(x)]$  for  $x \in \{0; 15\}$ 
  - Encryption  $\rightarrow$  TCAM
  - Decryption  $\rightarrow$  Memory

# Shared vs separated match line

Match line		Shared (1)	Separated (n)
Search time		1 address per clock cycle	1 clock cycle
Implementation constraint		RNG (security purpose) + counter, time constant ?	-
Input Controller	area	Medium	small
Output Controller	area	Small	high
Energy consumption		Variable to constant	High but constant


# Photon-Beetle Sbox

## Memory mode (*Sbox*)

 

address	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Read value	C	5	6	B	9	0	A	D	3	E	F	8	4	7	1	2
 
## TCAM mode ( $Sbox^{-1}$ ) : Shared ML, search value = 0



# Agenda

---

1. Introduction
2. Ferroelectric field effect transistor
3. TC-MEM memory and Sbox implementation
4. Non-volatile logic gates and operators for security
5. Conclusion




# Hardware desing

- We define a non-volatile logic gate  $\boxplus$  with one input  $A$  and one output  $Y$ ;
- This gate perform a logical function symbolised with the operator  $\circ (\cdot, +, \oplus)$  ;
- It contains a preprogrammed value  $X$  include in  $GF(2) = \{0,1\}$  and perform the following operation :


$$Q = A \circ X ;$$

- Its symbol is :

 


# Hardware desing


- AND gate :

 

- OR gate :

 

- XOR gate :

 

# Non-volatile GF(2<sup>4</sup>) adder

- Adding in GF(2<sup>m</sup>) corresponds to a bit XORing

 


Fig. 2 : Porte XOR en FeFET<sup>1</sup>

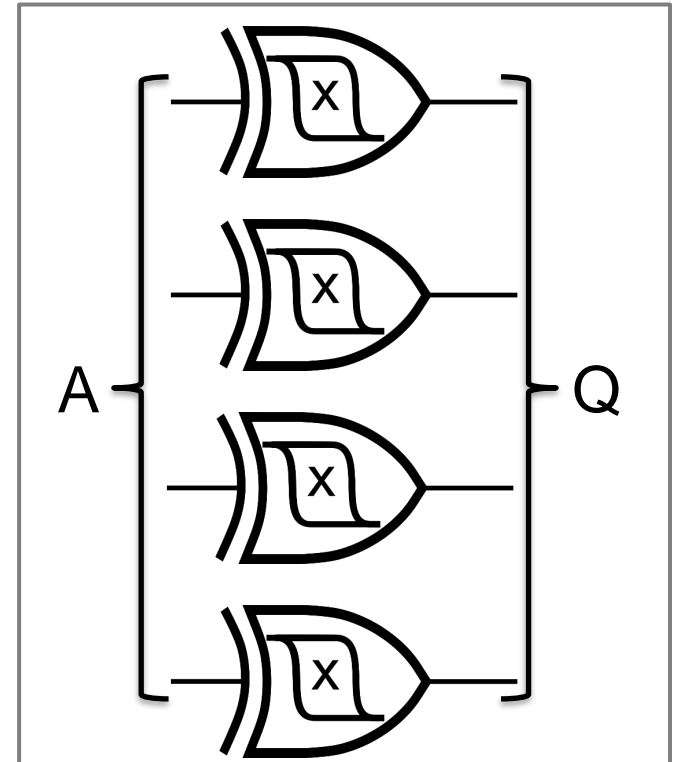


Fig. 3 : Non-volatile adder.

<sup>1</sup>C. Marchand, I. O'Connor, M. Cantan, E. T. Breyery, S. Slesazecky and T. Mikolajick, "FeFET based Logic-in-Memory: an overview", DTIS 2021.

# GF(2<sup>4</sup>) multiplier

- Two architectures possible:
  - Combinatory (need more component)
  - Sequential (with a complexity depending of the size-bit; O(n))

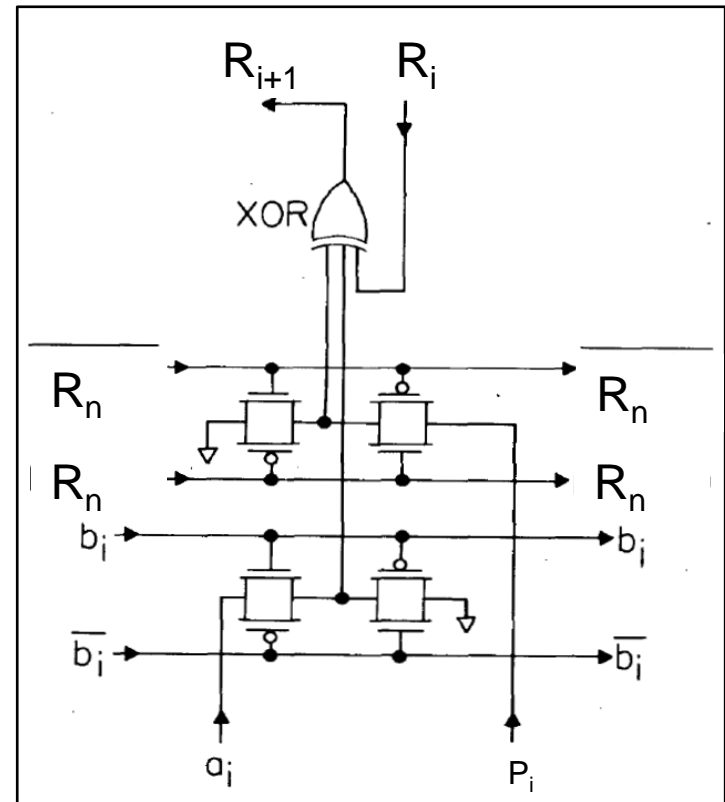


Fig. 4 : 1-bit Galois field multiplier<sup>1</sup>.

<sup>1</sup>P. A. Scott, S. E. Tavares, L. E. Peppard, "A Fast VLSI Multiplier for GF(2<sup>m</sup>)", *IEEE Journal on Selected Areas in Communications*, Vol. 4, Issue 1, January 1986.

# Non-Volatile GF(2<sup>4</sup>) multiplier

- Store irreducible polynomial
- Store one constante ?

 


Fig. 5 : Porte AND en FeFET


 


Fig. 6 : 1-bit Galois field multiplier
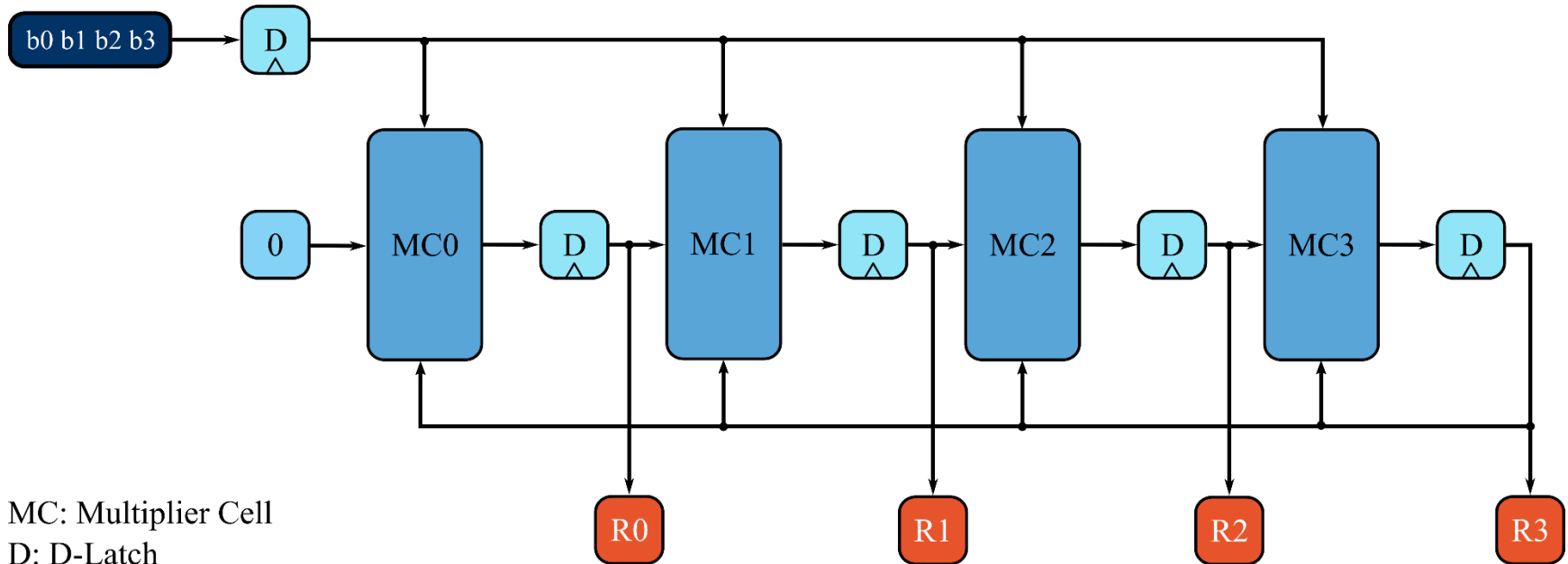
# Non-Volatile GF(2<sup>4</sup>) multiplier



MC: Multiplier Cell  
D: D-Latch

Fig. 7 : Non-volatile 4-bits Multiplier architecture.

# Conclusion

## The TC-MEM:

1. New memory circuit accessible by address and by content
2. Can be used to implement cryptographic Sbox with high area and energy efficiency
3. Serial implementation seems to be more interesting for security

## Non-volatile logic gates :

1. Can be used to implement specific operation storing constants :
  1. Adder
  2. Multiplier, ...

## Future works :

1. Implement all these operations in a RISC-V environment
2. Design an ASIC to validate and evaluate the operators
3. ...

# Thank you for your attention



This work has been carried out using the framework of the SECRET project supported by the French “Agence Nationale de la Recherche” under project number ANR-20-CE39-0006.